

# Assignment - 6

(Ques 15)  
Adwait Noravane  
PH3104.

1. Silicon diode 1N2615 - -  
 $I_s = 10 \mu A$ ,  $T = 22^\circ C = 295 K$ ,

$$i_D = i_s \left( \exp\left(\frac{V_D}{\eta V_T}\right) - 1 \right), \quad \eta = 2 \text{ for silicon diode.}$$

$$V_T = \frac{T}{11600} = \frac{295}{11600} \approx 25.43 \text{ mV.}$$

(a) ~~graph in~~ plot in zip.

(b)  $i_{D \max} = 750 \text{ mA}$ .

$$\ln\left(\frac{i_D}{I_s}\right) \approx \frac{V_D}{V_T} \Rightarrow (V_D)_{\max} = V_T \times \ln\left(\frac{i_{D \max}}{I_s}\right)$$

$$= 0.02543 \times \ln\left(\frac{750 \times 10^{-3}}{10^{-5}}\right)$$

$$= 570.8 \text{ mV}$$

(c)  $T = 22^\circ C = 295 K$ ,  $T = 72^\circ C = ?$   
 $i_s = 10^{-5}$

As it doubles every  $10^\circ C$  rise.

$$I_s' = I_s \times 2^{\frac{T_f - T_i}{10}} = 10^{-5} \times 2^5$$
$$= 320 \mu A.$$



2. (a) ideal - half wave rectifier.

For ideal half wave,

output  

$$V(t) = \begin{cases} V_{in}(t), & V_{in}(t) > 0 \\ 0, & V_{in}(t) \leq 0 \end{cases}$$

$$V_{in} = A \sin(\omega t).$$

Fourier coefficients:-

$$a_k = \frac{1}{T} \int_0^T V(t) e^{-ik\omega t} dt = \frac{A}{T} \int_0^{T/2} \frac{e^{i\omega t} - e^{-i\omega t}}{2i} e^{-ik\omega t} dt$$

$$= \frac{A}{2iT} \int_0^{\pi/\omega} (e^{i\omega(1-k)t} - e^{-i\omega(1+k)t}) dt$$

$$= \frac{A}{2iT} \left[ \frac{e^{i\omega(1-k)t}}{i\omega(1-k)} + \frac{e^{-i\omega(1+k)t}}{i\omega(1+k)} \right]_0^{\pi/\omega}$$

$$= \frac{-A}{4\pi} \left( \frac{e^{i(HK)\pi} - 1}{(1-k)} + \frac{e^{-i(HK)\pi} - 1}{(1+k)} \right)$$

$$a_k = \frac{A}{2\pi} \left( \frac{(-1)^k + 1}{1-k^2} \right) \quad \text{for } k \neq \pm 1$$

~~for  $k = \pm 1$~~

~~$a_1 = A$~~   
 for  $k = +1$   

$$a_1 = \frac{A}{2\pi} \left( \frac{\frac{d}{dk} (e^{-ik\pi} + 1)}{\frac{d}{dk} (1-k^2)} \right) = -\frac{iA}{4}$$

$$V(t) = \sum_{k=-\infty}^{\infty} \frac{A}{2\pi} \left( \frac{(-1)^k + 1}{1-k^2} \right) e^{ik\omega t}$$

(b) ideal full wave rectifier.

$$V(t) = |V_{in}(t)|$$

let

$$\omega = \frac{2\pi}{T}$$

$$V_{in} = A \sin \omega t$$

let  $\omega = \frac{2\pi}{T}$ ,  $\omega_0 = \frac{2\pi}{T_0}$ , with  $T_0 = \frac{1}{2}T$ ,  $\omega_0 = 2\omega$

$$a_k = \frac{1}{T_0} \int_0^{T_0} V(t) \cdot e^{-ik\omega_0 t} dt$$

$$= \frac{A}{2T} \int_0^{T_0} \sin \omega t \cdot e^{-ik\omega_0 t} dt = \frac{A}{2iT_0} \int_0^{T_0} e^{i\omega(\frac{1}{2}-k)t} - e^{-i\omega(\frac{1}{2}+k)t} dt$$

$$= \frac{-A\omega}{4\pi} \left[ \frac{e^{2\pi(\frac{1}{2}-k)t}}{i\omega(\frac{1}{2}-k)} + \frac{e^{-i\omega(\frac{1}{2}+k)t}}{i\omega(\frac{1}{2}+k)} \right]_0^{2\pi/\omega_0}$$

$$= -\frac{A}{4\pi} \left[ \frac{(1 + e^{-2\pi ik})}{-k^2 + \frac{1}{4}} \right]$$

$$= \frac{2A}{\pi(1-4k^2)}$$

$$\underline{a_0 = \frac{2A}{\pi}}$$

$$V(t) = \sum_{k=-\infty}^{\infty} \frac{2A}{\pi(1-4k^2)} e^{ik\omega_0 t}$$



3) (a)  $I = i_{dc} + i_r$

$$\langle I^2 \rangle = \frac{1}{T} \int_0^T I^2 \omega \omega ds$$

$$= \frac{1}{T} \int_0^T (I_{dc}^2 + I_r^2 + 2I_{dc}I_r) dt$$

$$= \langle I_r^2 \rangle + \underbrace{I_{dc}^2}_{\uparrow \text{dc}} + \frac{2I_{dc}}{T} \int_0^T I_r dt$$

$$\int_0^T I_r dt = \int_0^T \left[ \sum_{n=1}^{\infty} \frac{\cos(n\omega t)}{(1-4n^2)\pi} + \int_0^{\pi} \frac{I_p}{2} \sin \omega t dt \right]$$

as above

$$= \sum_{n=1}^{\infty} \frac{\sin 4n\pi}{(1-4n^2)\pi} - \frac{\frac{I_p}{2} \cos \omega t}{\uparrow 0} \Big|_0^T$$

$$= 0$$

$$\Rightarrow \langle I^2 \rangle = \langle I_r^2 \rangle + I_{dc}^2$$

$$I_{ac}^2 = \langle I_r^2 \rangle$$

$$I = \sqrt{I_{dc}^2 + I_{ac}^2}$$

$$r = \frac{I_{ac}}{I_{dc}} \dots \text{ripple factor} = \sqrt{\frac{I^2}{I_{dc}^2} - 1}$$

$$I_{dc} = \frac{1}{2\pi} \int_0^{\pi} I_p \sin \alpha d\alpha = \frac{I_p}{\pi}$$

$$I = \left( \frac{1}{2\pi} \int_0^{\pi} I_p^2 \sin^2 \alpha d\alpha \right)^{1/2} = \frac{I_p}{2}$$

$$\Rightarrow r = \sqrt{\frac{\pi^2}{4} - 1} = 1.21$$

for half wave rectifier


$$I = \left( \frac{1}{\pi} \int_0^{\pi} I_p^2 \sin^2 \alpha \, d\alpha \right)^{1/2} = \frac{I_p}{\sqrt{2}}$$

$$I_{ac} = \frac{1}{\pi} \int_0^{\pi} I_p \sin \alpha \, d\alpha = \frac{2I_p}{\pi}$$

$$\Rightarrow r = \sqrt{\frac{I_p^2}{8} - 1} = 0.483$$

} Full wave rectifier


4. correct config-

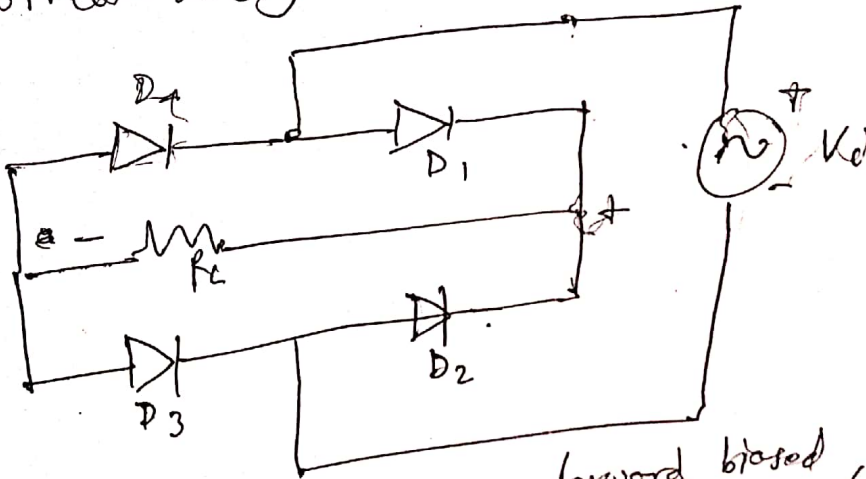

For  $V_i > 0$ ,  $D_1$  &  $D_3$  are forward biased, we get DC output  
 $V_o = \frac{2V_i}{\pi}$

For  $V_i < 0$ ,  $D_2$  &  $D_4$  are forward biased and we get DC output  
 $V_o = \frac{2V_i}{\pi}$  in the other direction

Wrong configs:

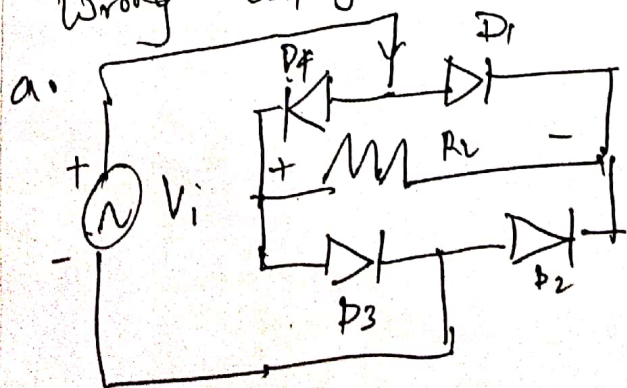

No output through  $R_L$

Here current flows through both  $D_1$  &  $D_4$ .  
 $D_2$  is reverse biased, so no current through it.


Current through  $D_2$  &  $D_3$  with output  
 $V_o = 0$  for  $V_i > 0$ .

as ~~current~~ current can't divide as ideal diodes offer no resistance.

$V_o = 0$  for  $V_i < 0$  as current can't flow.



b.

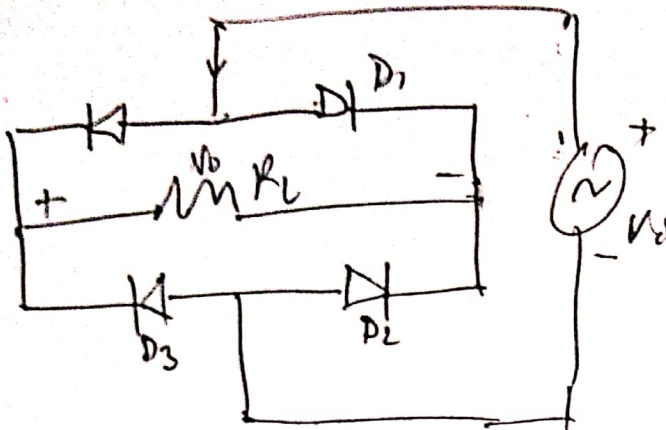


No output over  $R_L$ .

For  $V_i > 0$ ,  
 $D_1$  &  $D_4 \Rightarrow$  forward biased.  
 $D_3$  &  $D_2 \Rightarrow$  reverse biased.  
 $\Rightarrow$  No current.

$V_o = 0$ .  
 for  $V_i < 0$   
 $V_o = 0$  too.

c.

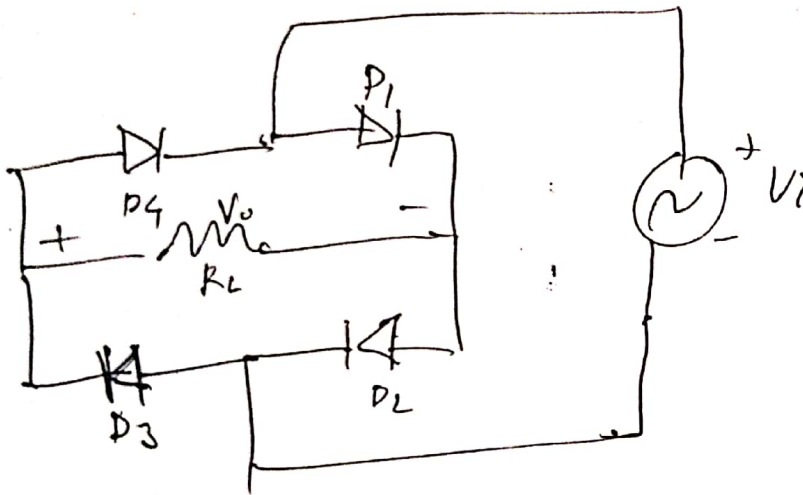

no output over  $R_L$ .


For  $V_i > 0$ ,  
 Current through  
 $D_1$  &  $D_2$ .

$\Rightarrow V_o = 0$

For  $V_i < 0$ ,  
 Current through  
 $D_3$  &  $D_4$ .

$\Rightarrow V_o = 0$

d)

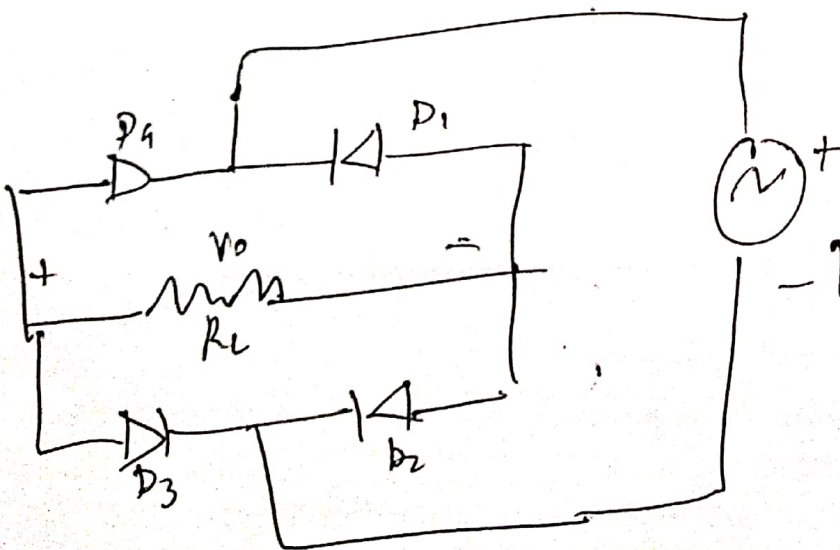

No output


For  $V_i > 0$ ,  
 $D_1$  &  $D_4 \Rightarrow$  reverse biased

No output.

For  $V_i < 0$ ,  
 $D_2$  &  $D_3 \Rightarrow$  reverse biased

No output


e)

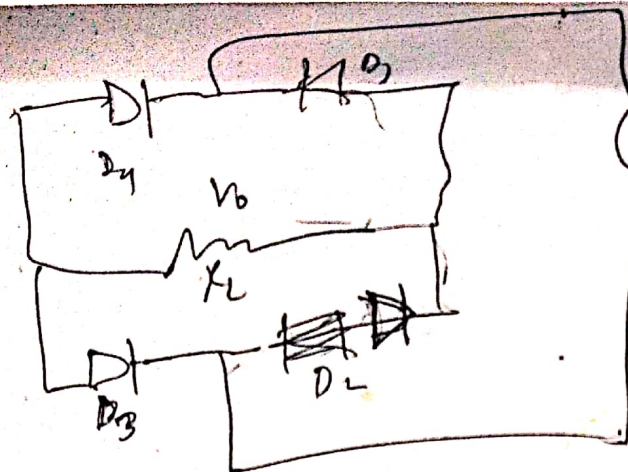

No output

$V_i < 0$   
 current over  $D_1$  &  $D_2$   
 $V_i > 0$   
 $D_1$  &  $D_4 \Rightarrow$  reverse


f)

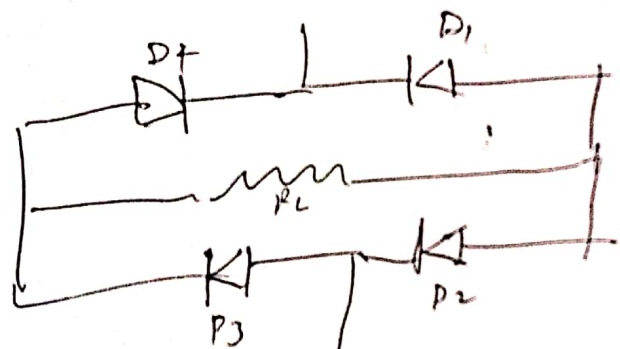

No output

$V_i > 0 \Rightarrow$  no current  
 $V_i < 0 \Rightarrow$  current over  $D_3$  &  $D_4$  only.

g)

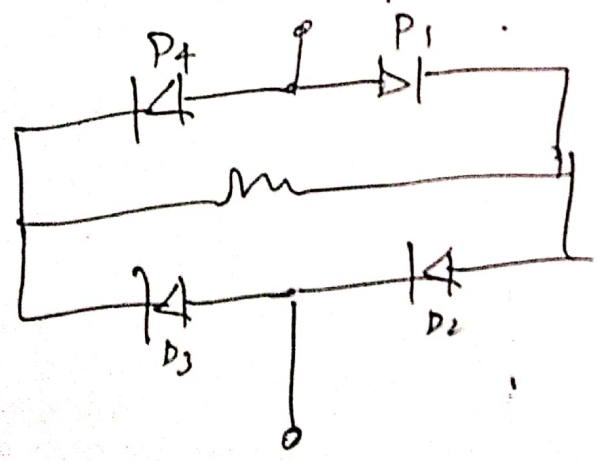

No output

$V_i > 0$   
 current over  $D_1$  &  $D_2$ .  
 $V_i < 0$   
 No current flow

Q5  $V_1 = 220 \text{ V}$

$$\frac{N_1}{N_2} = \frac{20}{1}$$

$$\text{max power} = 220\sqrt{2} \text{ V.}$$

Secondary voltage,  $V_o = \frac{220\sqrt{2}}{20} = 11\sqrt{2} \text{ V} = \text{Centre tapped} = V_m = \frac{11\sqrt{2}}{2} \text{ V.}$

$$I_{dc} = \frac{2I_m}{\pi}$$

$$V_{DC} = \frac{2V_m}{\pi} = \frac{9.9}{2} \text{ V.} = \frac{22\sqrt{2}}{2\pi} = 4.95 \text{ V.}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{11}{2} \text{ V} = 5.5 \text{ V}$$

Peak inverse voltage,  $V_p = 22\sqrt{2} = \frac{31.11 \text{ V.}}{2} = \underline{\underline{15.55 \text{ V.}}}$