

## PH3104 Problem Set 6

**Q 1)** A 1N2615 silicon diode has a reverse saturation current  $I_s$  of  $10\mu\text{A}$  at  $22^\circ\text{C}$ .

(a) Plot the diode current against voltage at this temperature (choose a reasonable range for the voltage).

(b) This diode has a maximum dc current rating of 750 mA. Determine the maximum safe forward voltage that it can be subjected to.

(c) What is the expected reverse saturation current at  $72^\circ\text{C}$ ?

(You may have to look up relevant parameter values on the net.)

**Q 2)** Work out the Fourier series for the output from (a) an ideal half wave rectifier, and (b) an ideal full wave rectifier.

**Q 3) a)** The current output of a rectifier can be expressed as  $I = I_{\text{dc}} + I_r$ . Show that

$$\langle I^2 \rangle = \langle I_r^2 \rangle + I_{\text{dc}}^2$$

where the  $\langle \dots \rangle$  denote average over time.

b) Use this Derive the expressions for the ripple factor for both the ideal full wave and half wave rectifier.

**Q 4)** The diodes in a bridge rectifier are connected in a particular way. Discuss the different ways in which you can connect the diodes *wrongly* (I mean reverse the p and the n side), and describe the output through the resistance in each case. Assume that all the diodes are ideal.

*Hint : reversing all the diodes does not count as a wrong connection - can you see why?*

**Q 5)** A full wave rectifier is connected to the 220 V ac mains by a 20:1 step down transformer with a center tap. Determine the peak, dc and rms values of the output, assuming that the diodes are ideal.